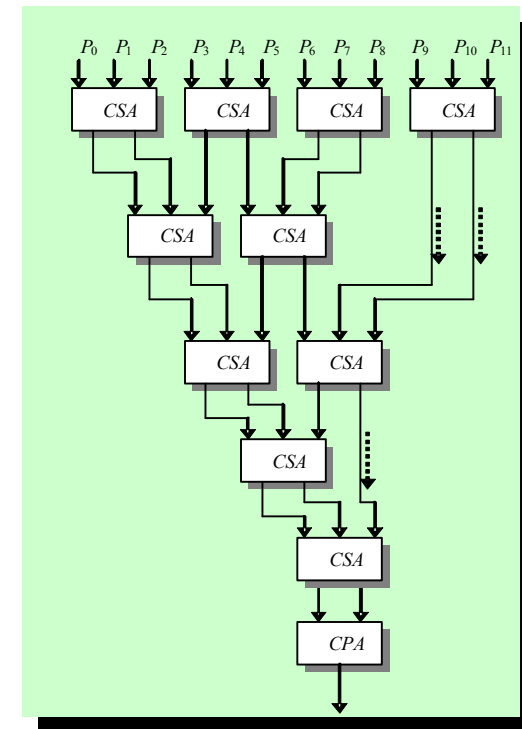


Digital Integrated Circuit Design

Lecture 12 – Building Blocks (Adders)



Adib Abrishamifar
EE Department
IUST

Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Outline

- ▶ **Types of logic circuit**
 - ▶ Combinational
 - ▶ Sequential
- ▶ **Design methods**
 - ▶ Gate level design
 - Example: Full adder
 - ▶ Block level design
 - Example: Parallel adder, ALU
- ▶ **Propagation Delay**

Outline

▶ Building Blocks for Digital Architectures

▶ Arithmetic unit

- Bit-sliced datapath (**Adders**, Multipliers, Shifters, Comparators, etc.)

▶ Memory

- RAM, ROM, Buffers, Shift registers

▶ Control

- Finite state machine (PLA, random logic)
- Counters

▶ Interconnect


- Switches
- Arbiters
- Bus

Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders

► Half Adder (Gate-level Design)

 


X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

► $C = XY$

► $S = X'Y + XY' = X \oplus Y$

Adders

► Half Adder (Gate-level Design)

 


Adders

► Half Adder

- To add two binary numbers, we need to add 3 bits (including the carry)

$$\begin{array}{rcccccc} & & 1 & 1 & 1 & & \text{carry} \\ & & 0 & 0 & 1 & 1 & X \\ + & & 0 & 1 & 1 & 1 & Y \\ \hline & & 1 & 0 & 1 & 0 & S \\ \hline \end{array}$$

 - Need Full Adder (so called as it can be made from two half-adders)



Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders

► Full Adder (Gate-level Design)

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

► $C = XY + XZ + YZ$

► $S = X'Y'Z + X'YZ' + XY'Z' + XYZ$

		C			
	YZ	00	01	11	10
x					
0				1	
1			1	1	1

		S			
	YZ	00	01	11	10
x					
0			1		1
1		1		1	

Adders

► Full Adder

► Alternative formula using algebraic manipulation

- $C = XY + XZ + YZ$
- $= XY + (X + Y)Z$
- $= XY + ((X \oplus Y) + XY)Z$
- $= XY + (X \oplus Y)Z + XYZ$
- $= XY + (X \oplus Y)Z$


- $S = X'Y'Z + X'YZ' + XY'Z' + XYZ$
- $= X'(Y'Z + YZ') + X(Y'Z' + YZ)$
- $= X'(Y \oplus Z) + X(Y \oplus Z)'$
- $= X \oplus (Y \oplus Z) \text{ or } (X \oplus Y) \oplus Z$

Adders

► Full Adder


$$C = XY + (X \oplus Y)Z$$

$$S = (X \oplus Y) \oplus Z$$

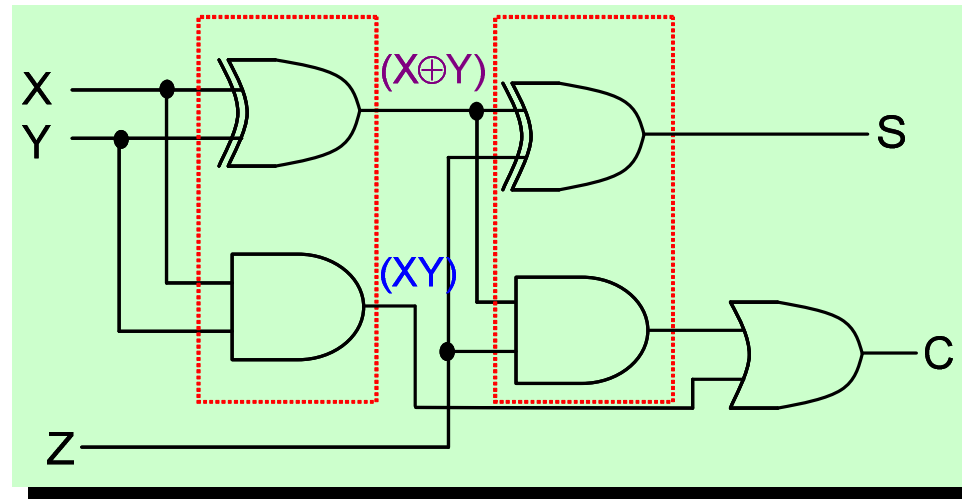


Adders

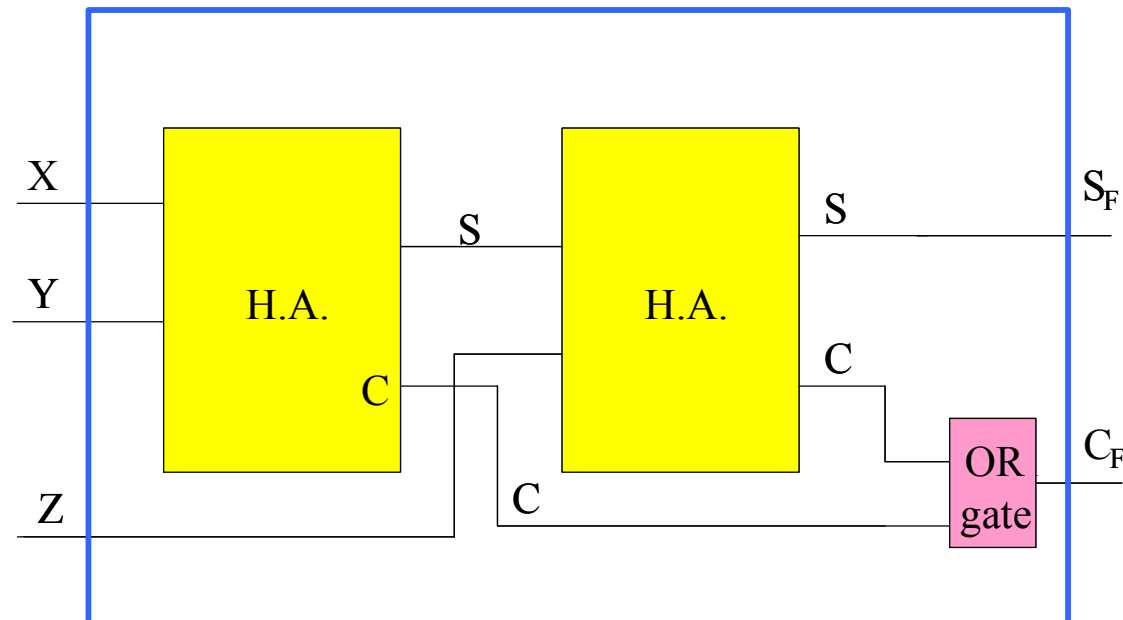- Full Adder made from two Half-Adders (+ OR gate)




Adders

► FA Gate Level (XOR FA, 16 Transistors)

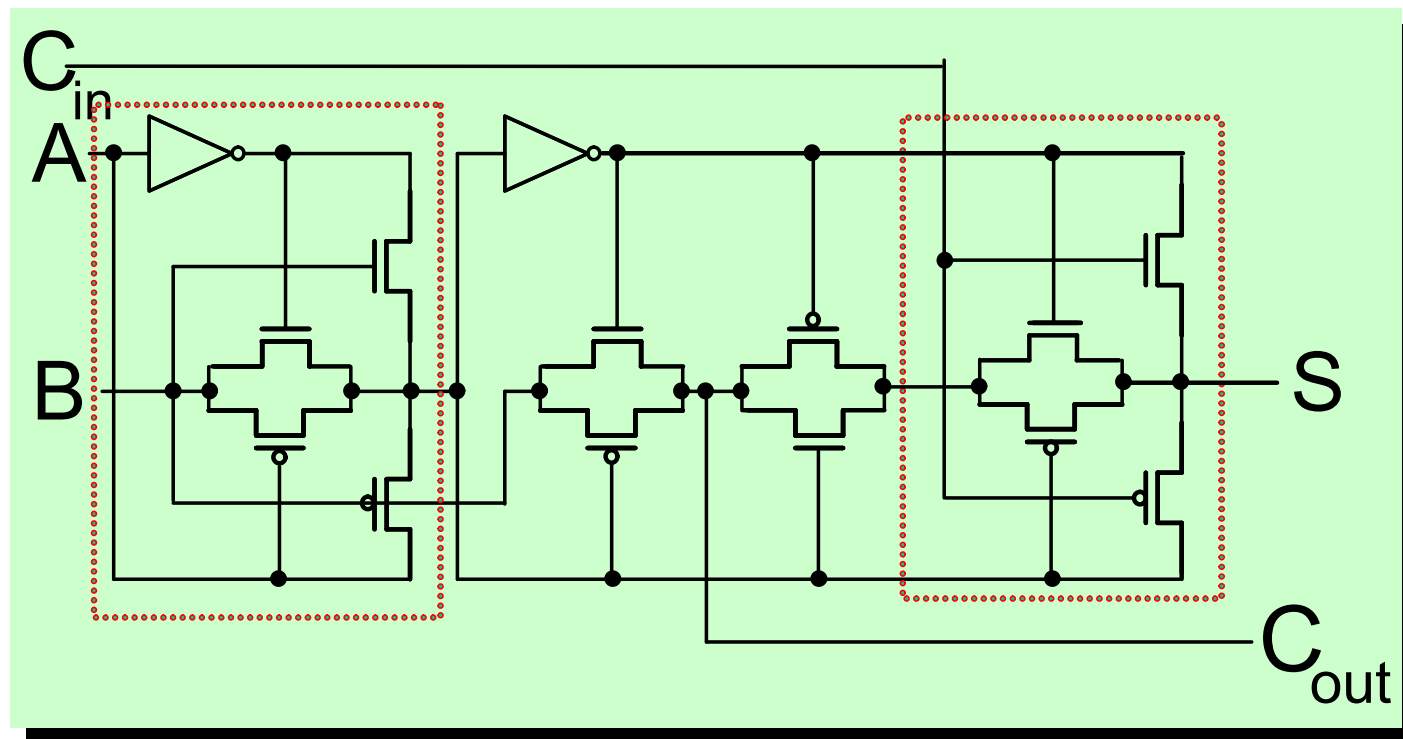




Adders

► CPL FA (20 + 8 transistors)

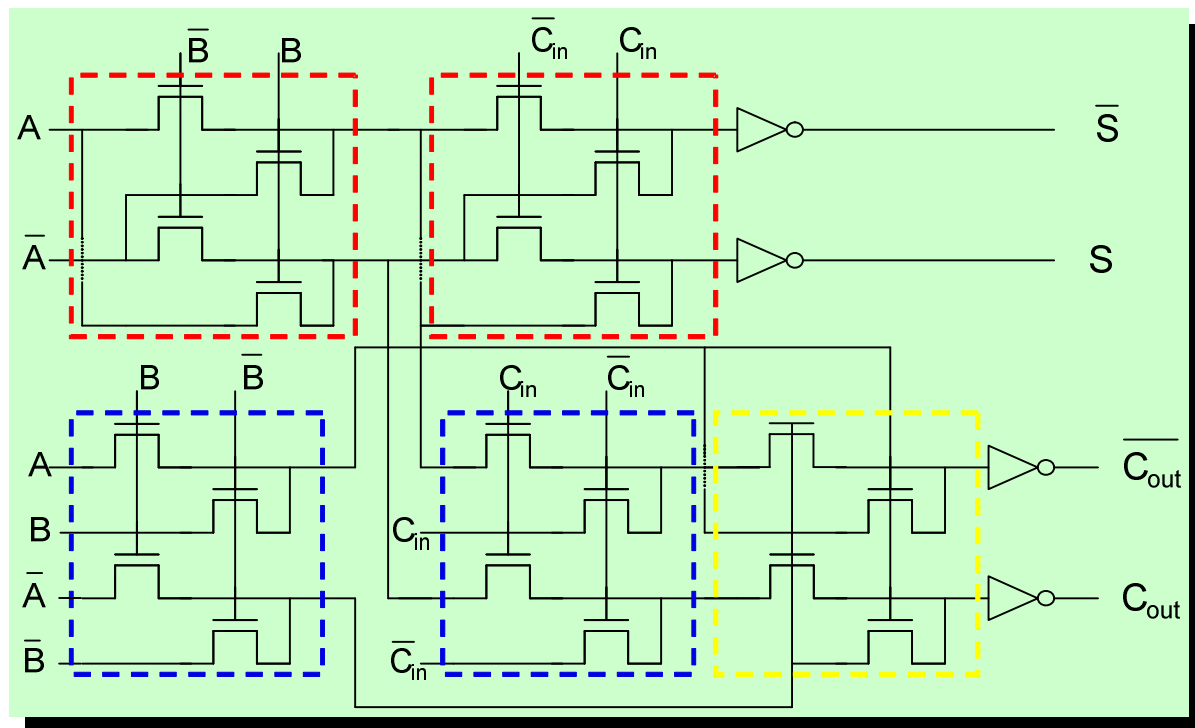


Adders

   
- Delay Balanced FA (Identical Delays for Carry and Sum, 20 +2 transistors)



Signal set-up

 


Carry generation

 

Sum generation

Adders

 - ▶ **N-bit adder called CPA (Carry Propagate Adder)**
 - ▶ Each sum bit depends on all previous carries
 - ▶ How do we compute all these carries quickly?



$$\begin{array}{r} \textcircled{0}000\textcircled{0} \\ 1111 \\ +0000 \\ \hline 1111 \end{array}$$

Carry propagation example 1: C_{in} and C_{out} are both 0.

$$\begin{array}{r} \textcircled{1}111\textcircled{1} \\ 1111 \\ +0000 \\ \hline 0000 \end{array}$$

Carry propagation example 2: C_{in} and C_{out} are both 1. The sum output is 0000, and the carry output is 1.


carries
 $A_{4...1}$
 $B_{4...1}$
 $S_{4...1}$

Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders

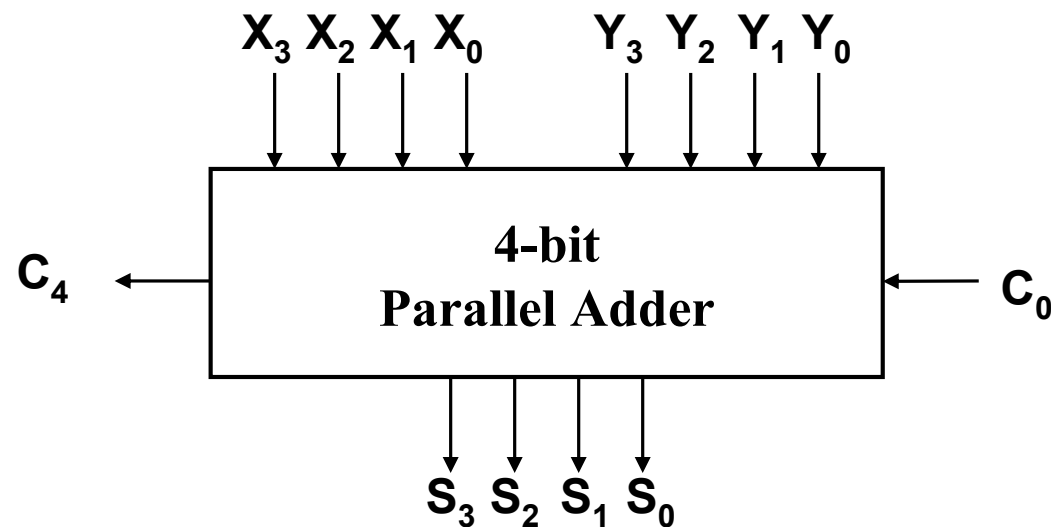- ▶ **Ripple-Carry Adder (Parallel Adder)**
 - ▶ Consider a circuit to add two 4-bit numbers together and a carry-in, to produce a 5-bit result



Adders


► Ripple-Carry Adder (Parallel Adder)

► Simplest design: cascade full adders

- Critical path goes from C_{in} to C_{out}
- Design full adder to have fast carry delay
- Addition formulae for each pair of bits (with carry in), has the same function as a full adder
- $C_{i+1} = X_i Y_i + (X_i \oplus Y_i) C_i$
- $S_i = X_i \oplus Y_i \oplus C_i$


Adders

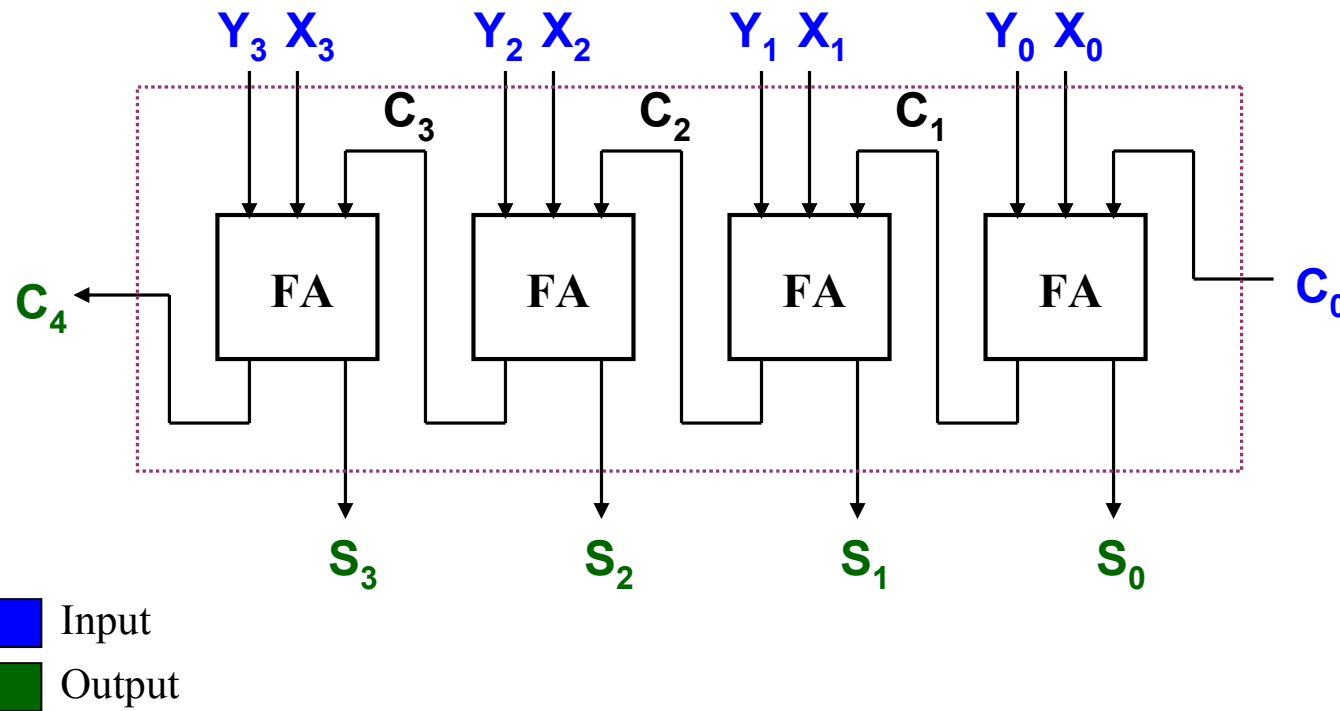- ▶ **Ripple-Carry Adder (Parallel Adder)**
 - ▶ Cascading 4 full adders via their carries




Adders

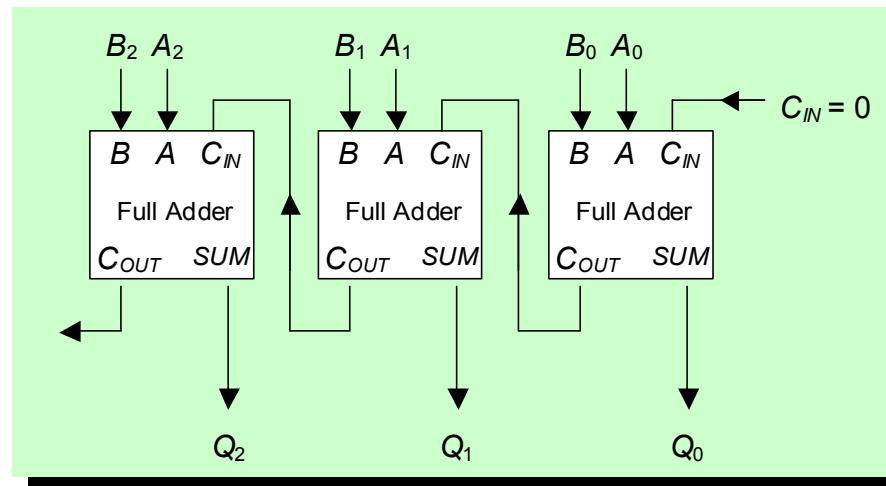- ▶ **Ripple-Carry Adder (Parallel Adder)**
 - ▶ Note that carry propagated by cascading the carry from one full adder to the next
 - ▶ Called **Parallel Adder** because inputs are presented simultaneously (in parallel)



Adders

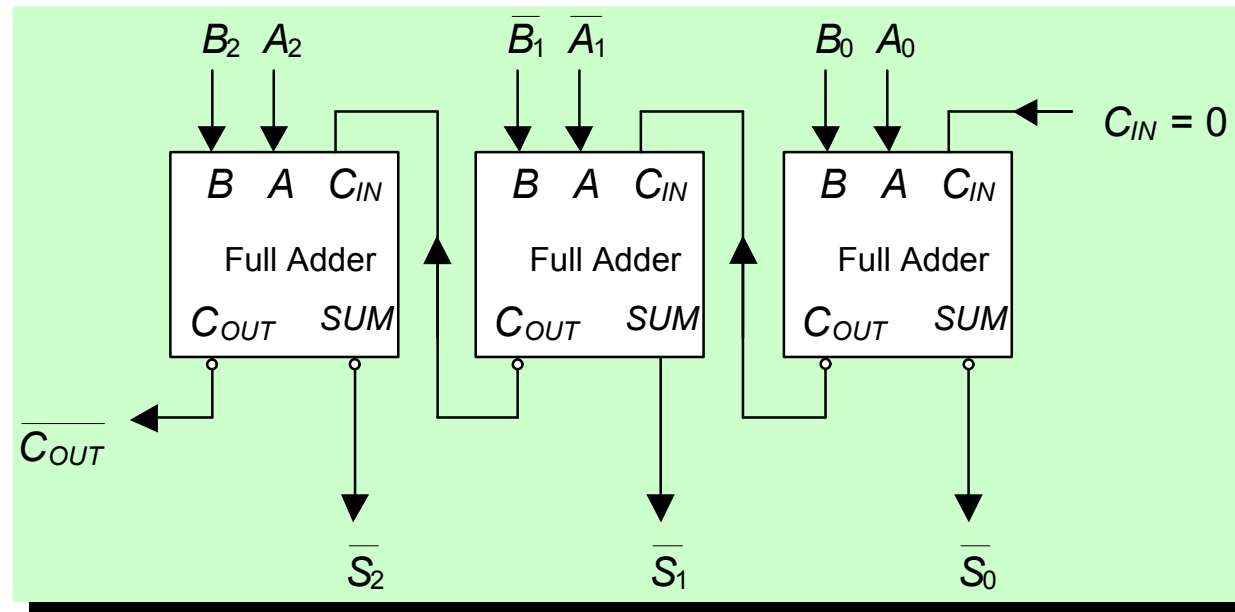
- ▶ **Ripple-Carry Adder (Parallel Adder)**
 - ▶ **Output Inverting (Carry-Sum)**



Adders

► Ripple-Carry Revisited

► $G_{i:0} = G_i + P_i \cdot G_{i-1:0}$

 


Adders

▶ How To Subtract ?

- ▶ Suppose added input to the adder that gave the one's complement of B
- ▶ What happens if set C_0 to 1 in the parallel adder?
- ▶ $\text{Sum} = A + B + 1$
- ▶ Then if select inverted B' , Sum is $A + B' + 1 = A + (B' + 1) = A + (-B) = A - B$
- ▶ Therefore can do subtract with the parallel adder if we add inverters and set C_0 to 1

Adders

► Subtraction

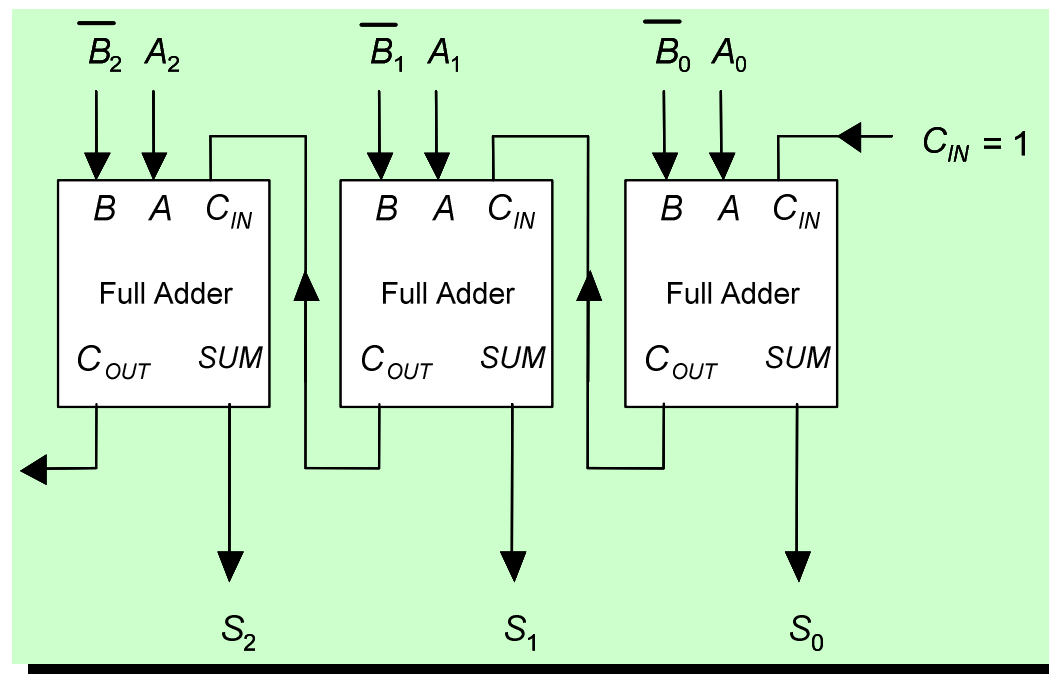


Adders

▶ Add / Sub Circuits Comparison

- ▶ Both the addition and subtraction circuits are based around the parallel adder
- ▶ For addition:
 - A and B are inputted directly to the adder
 - $C_{IN} = 0$
- ▶ For subtraction:
 - A is inputted directly
 - All the bits of B are complemented
 - $C_{IN} = 1$

Adders

► An Adder / Subtraction Circuit

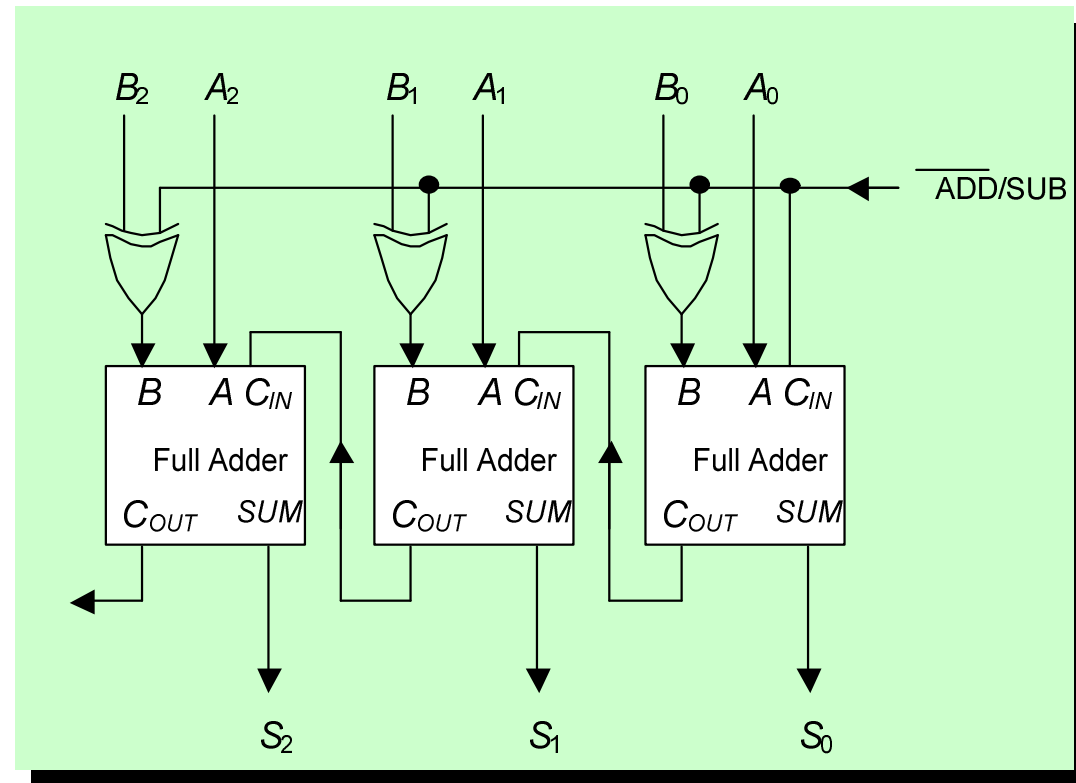

Adders

▶ Ripple-Carry Adder (Parallel Adder)

▶ Advantage:

- Simple logic, so small (low cost)

▶ Disadvantage:

- Slow ($O(N)$ for N bits) and lots of glitching (so lots of energy consumption)
- Propagation delay of ripple-carry parallel adders is proportional to the number of bits it handles
- Maximum Delay: $((n-1) \times 2 + 3)t$ (it is shown in near future!)


Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders


► Calculation of Circuit Delays

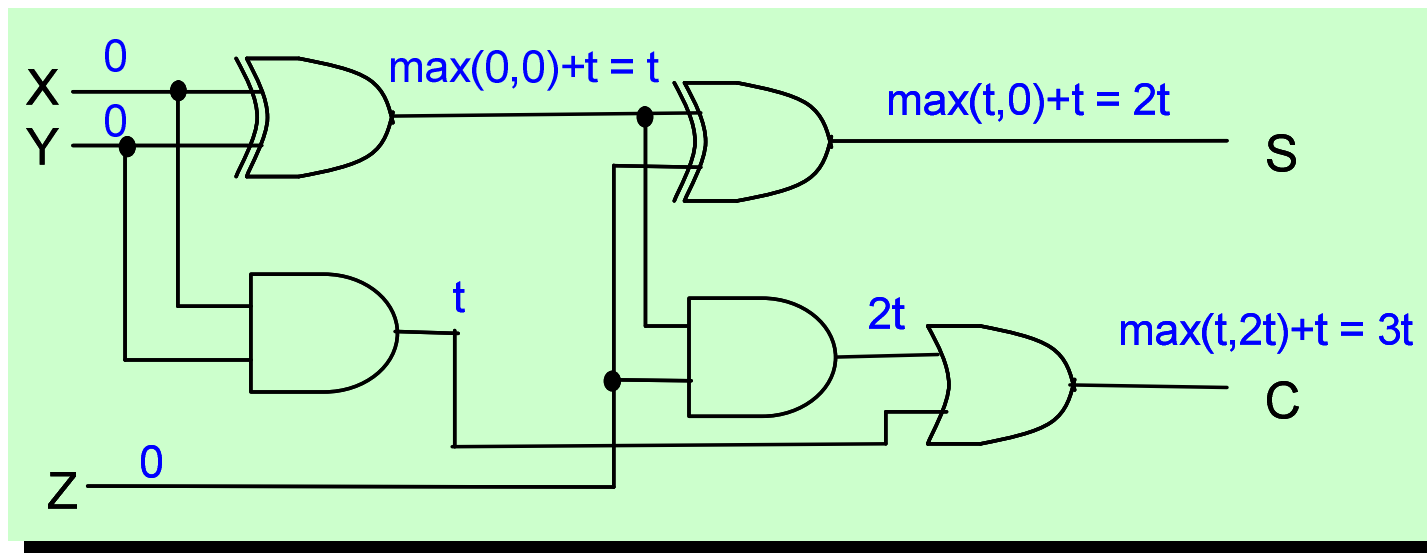- As a simple example, consider the full adder circuit where all inputs are available at time 0. (Assume each gate has delay t)




Adders

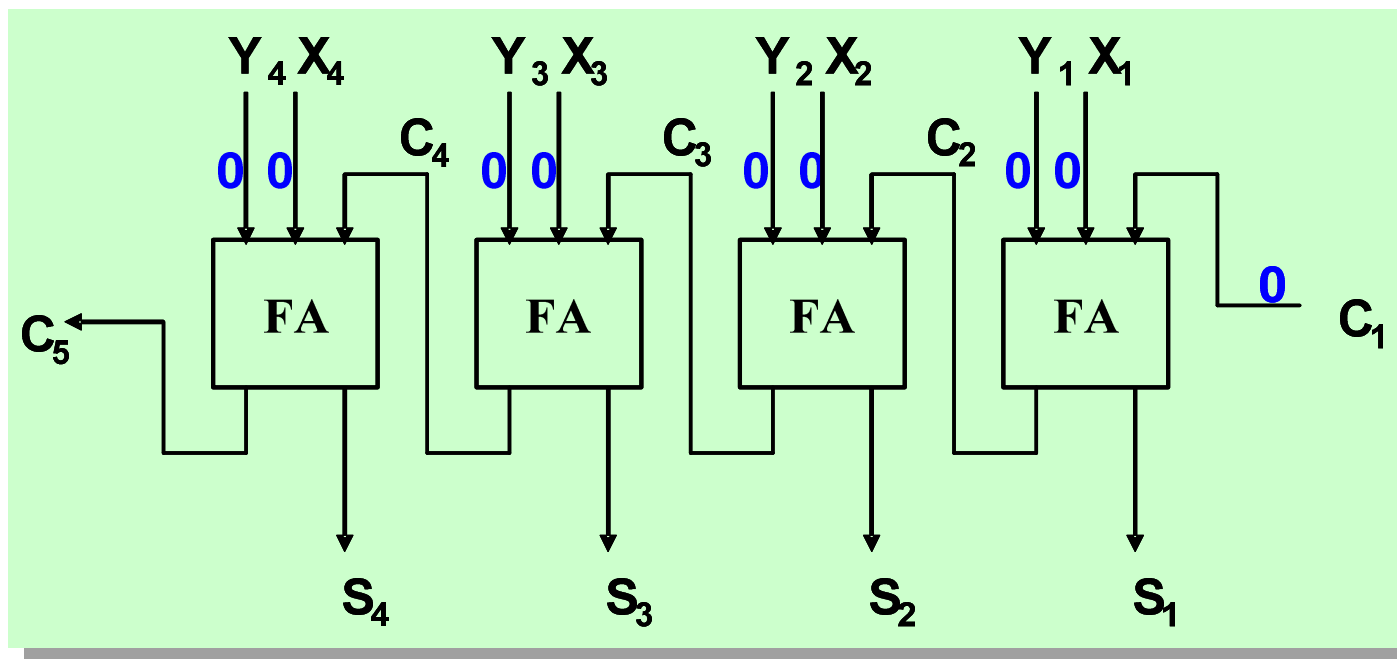- **Calculation of Circuit Delays**
 - More complex example: 4-bits parallel adder




Adders

 - ▶ **Calculation of Circuit Delays**
 - ▶ Analyze the delay for the repeated block
 - ▶ where X_i , Y_i are stable at 0t, while C_i is assumed to be stable at mt



Adders

► Calculation of Circuit Delays

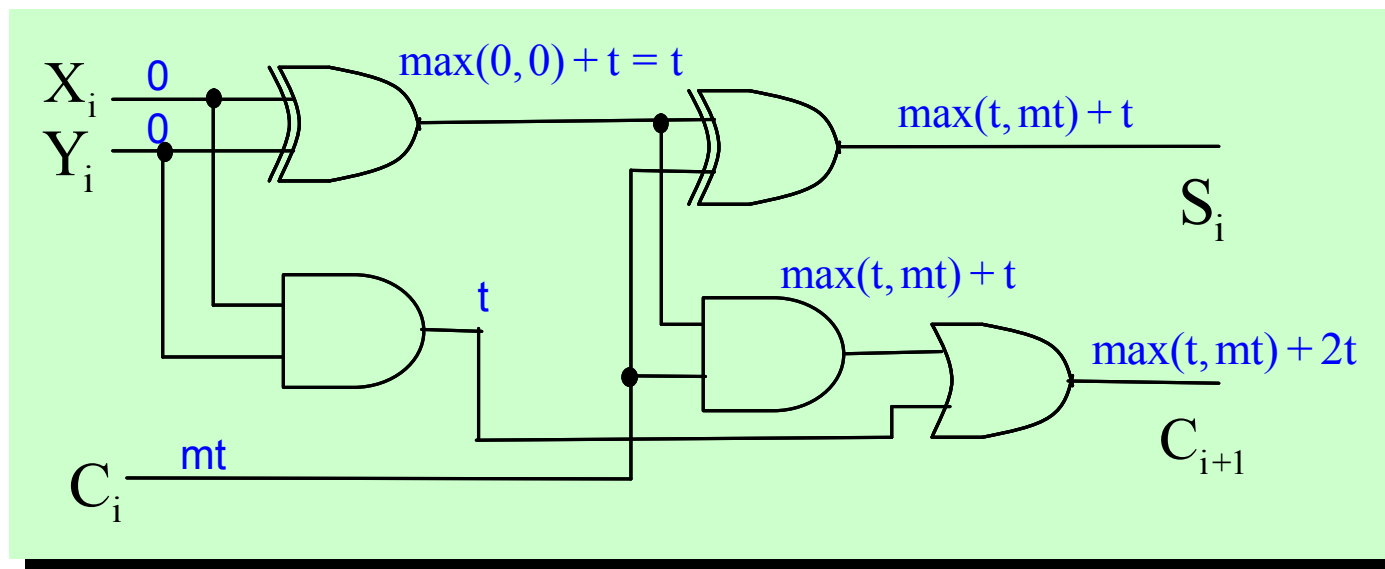

Adders

► Calculation of Circuit Delays

- ▶ When $i = 1$, $m = 0$: $S_1 = 2t$ and $C_2 = 3t$
 - ▶ When $i = 2$, $m = 3$: $S_2 = 4t$ and $C_3 = 5t$
 - ▶ When $i = 3$, $m = 5$: $S_3 = 6t$ and $C_4 = 7t$
 - ▶ When $i = 4$, $m = 7$: $S_4 = 8t$ and $C_5 = 9t$
-
- ▶ In general for an n -bit ripple-carry parallel adder
 - ▶ $S_n = ((n-1) \times 2 + 2)t$
 - ▶ $C_{n+1} = ((n-1) \times 2 + 3)t$

Adders


- ▶ **Ways of improving the speed**
 - ▶ **Use better technology (e.g. ECL faster than TTL gates)**
 - Faster technology is more expensive, needs more power, lower-level of integrations
 - Physical limits (e.g. speed of light, size of atom)
 - ▶ **Use gate-level designs to two-level circuits! (use sum-of-products/product-of-sums)**
 - Complicated designs for large circuits
 - Product/sum terms need MANY inputs!
 - ▶ **Use clever (other) techniques**

Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**


Adders

 - ▶ **Carry-Bypass Adder (Carry-Skip Adder)**
 - ▶ Carry-ripple is slow through all N stages
 - ▶ Carry-Bypass Adder allows carry to skip over groups of n bits
 - Decision based on n-bit propagate signal




Adders

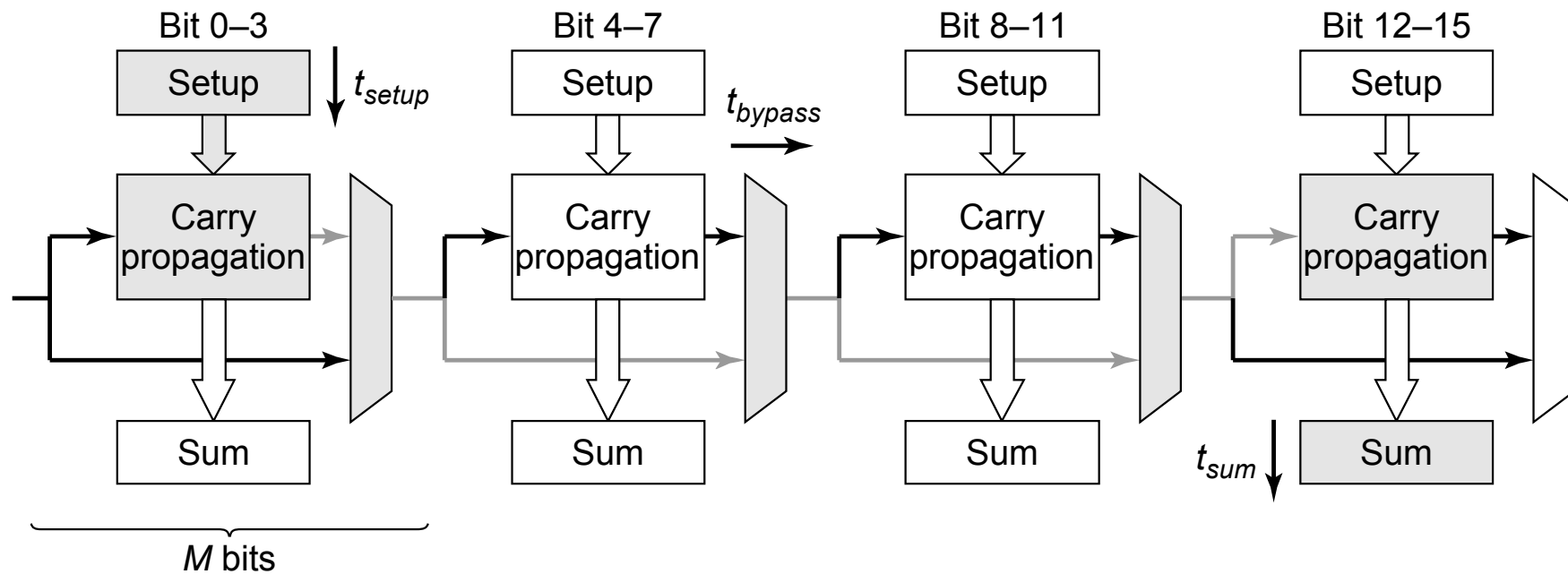- ▶ **Carry-Bypass Adder (Carry-Skip Adder)**
 - ▶ Carry-skip allows carry to skip over groups of m bits



Adders


► Carry-Bypass Adder (Carry-Skip Adder)

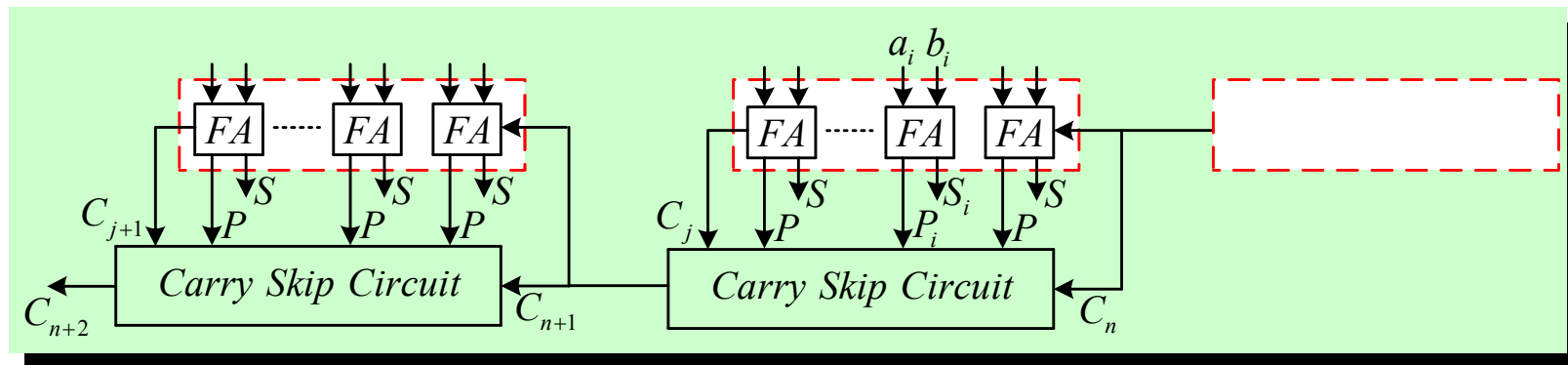

► $P_i = \text{XOR}(a_i, b_i)$

Adders

 
- ▶ **Carry-Bypass Adder (Carry-Skip Adder)**
 - ▶ Carry Skip Circuit
 - ▶ This Circuit calculate the carry for the next stage rapidly



Adders

► Carry-Bypass Adder (Carry-Skip Adder)

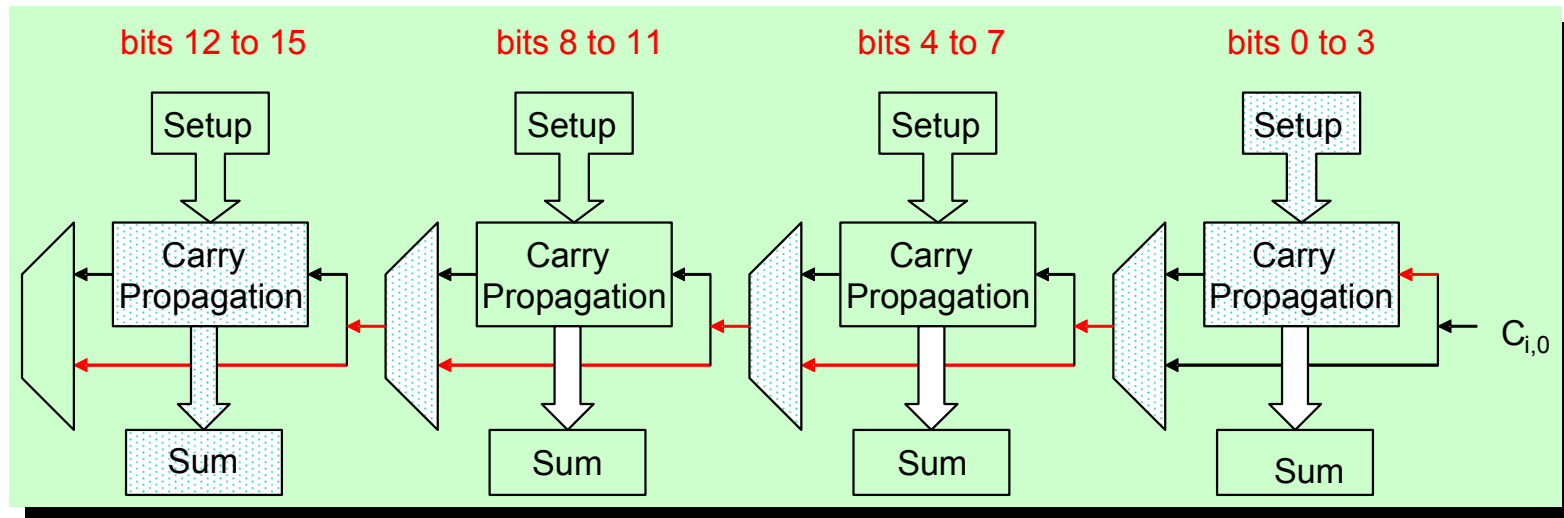- 4 (B)-bit Block
- Worst-case delay → carry from bit 0 to bit 15 = carry generated in bit 0, **ripples** through bits 1, 2, and 3, **skips** the middle two groups (B is the group size in bits), ripples in the last group from bit 12 to bit 15
- $T_{add} = t_{setup} + B t_{carry} + ((N/B) - 1) t_{skip} + B t_{carry} + t_{sum}$




Adders

► Carry-Bypass Adder (Carry-Skip Adder)

► Variable block sizes

 
- A carry that is generated in, or absorbed by, one of the inner blocks travels a shorter distance through the skip blocks, so can have **bigger blocks** for the inner carries without increasing the overall delay




Adders

► Inversion Property

 - Inverting all inputs to a FA results in inverted values for all outputs



≡

 


$$\bar{S}(A, B, C_{in}) = S(\bar{A}, \bar{B}, \bar{C}_{in})$$

$$\bar{C}_{out}(A, B, C_{in}) = C_{out}(\bar{A}, \bar{B}, \bar{C}_{in})$$

Adders

 - ▶ **Exploiting the Inversion Property**
 - ▶ Minimizes the critical path (the carry chain) by eliminating inverters between the FAs



Adders

► Fast Carry Chain Design

- The key to fast addition is a low latency carry network
- What matters is whether in a given position a carry is
- **generated** $G_i = A_i \& B_i = A_i B_i$
- **propagated** $P_i = A_i \oplus B_i$ (sometimes $A_i | B_i$)
- **annihilated (killed)** $K_i = \overline{A_i} \& \overline{B_i}$
- Giving a carry recurrence of $C_{i+1} = G_i | P_i C_i$

$$C_1 = G_0 | P_0 C_0$$

$$C_2 = G_1 | P_1 G_0 | P_1 P_0 C_0$$

$$C_3 = G_2 | P_2 G_1 | P_2 P_1 G_0 | P_2 P_1 P_0 C_0$$


$$C_4 = G_3 | P_3 G_2 | P_3 P_2 G_1 | P_3 P_2 P_1 G_0 | P_3 P_2 P_1 P_0 C_0$$

Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - [Manchester Carry Chain \(MCC\)](#)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**


Adders

 - ▶ **Manchester Carry Chain (MCC)**
 - ▶ Switches controlled by G_i and P_i
 - ▶ Total delay of
 - time to form the switch control signals G_i and P_i
 - setup time for the switches
 - signal propagation delay through N switches in the worst case




Adders

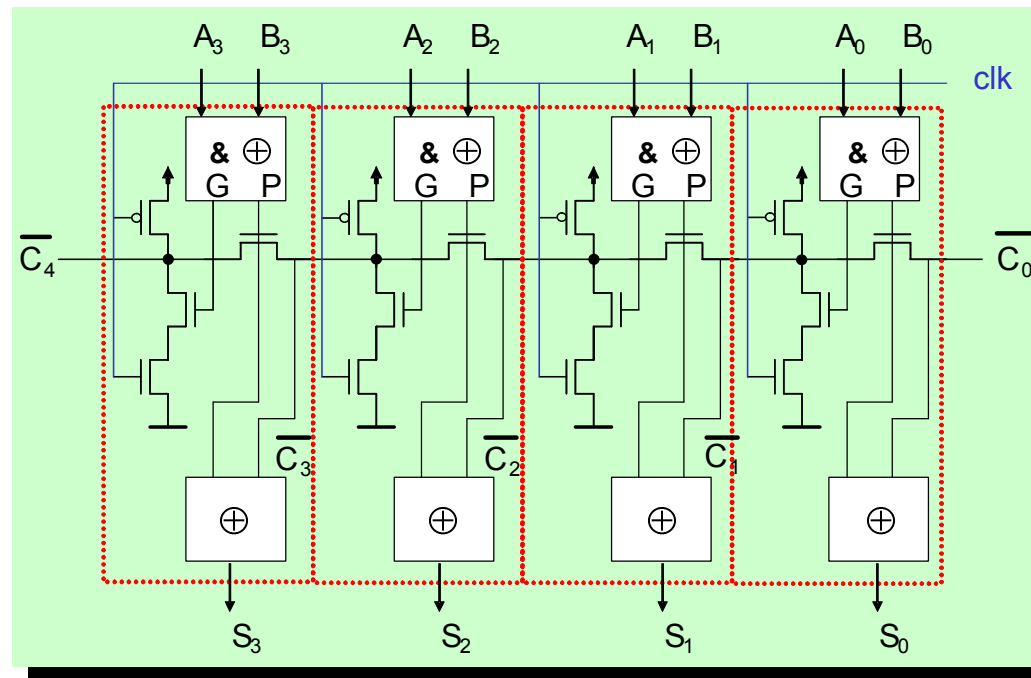- Manchester Carry Chain (MCC)
- 4-bit Sliced MCC Adder



Adders


► Manchester Carry Chain (MCC)

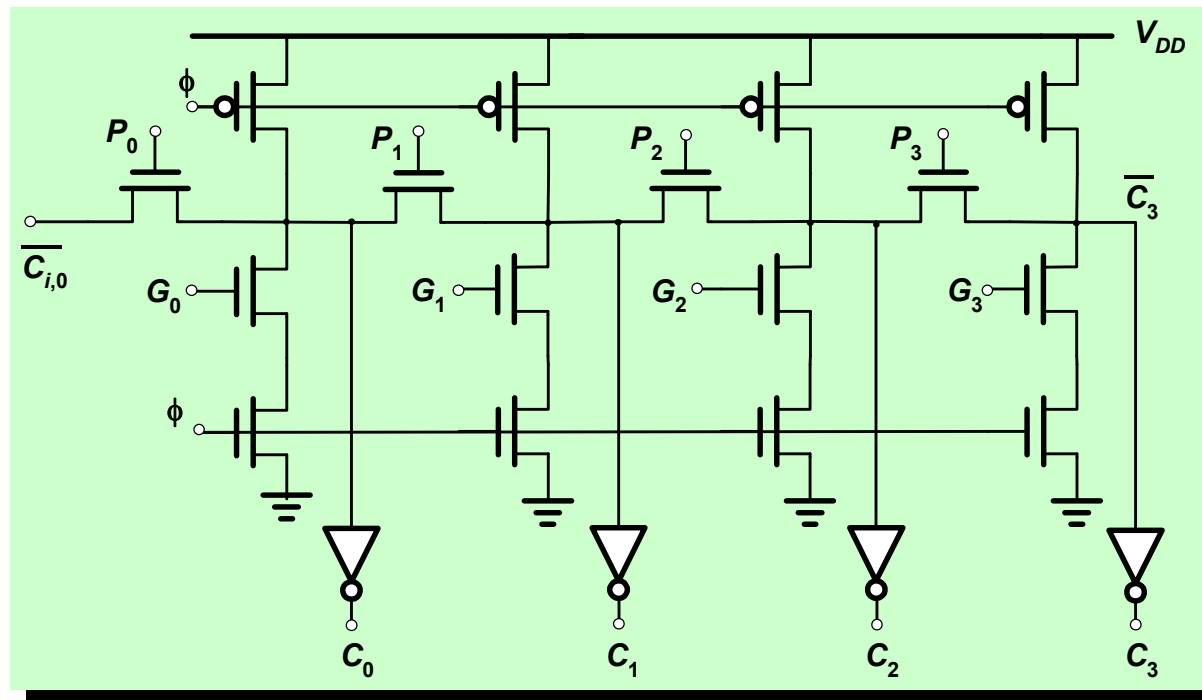

Adders

► Manchester Carry Chain (MCC)

► Stick Diagram

 


Contents


- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders

► Carry Select Adder

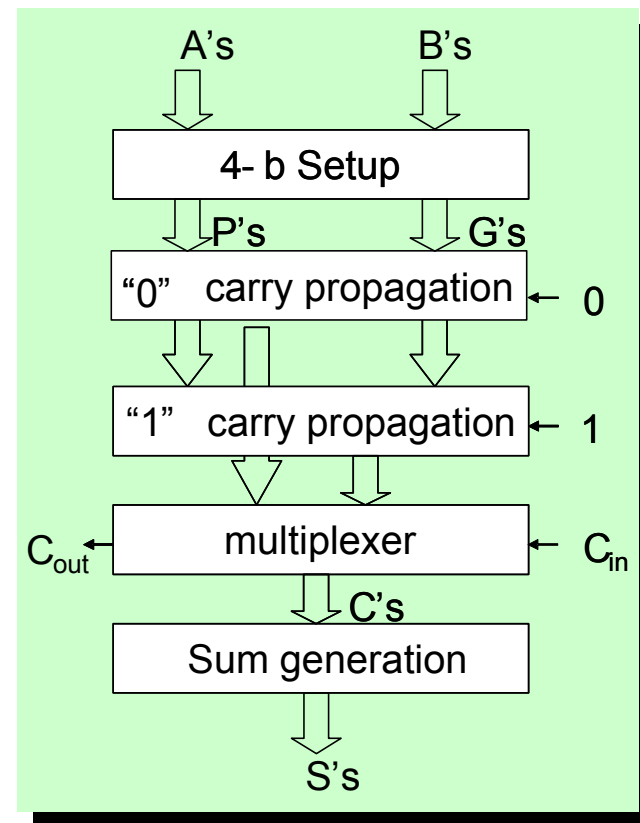- Trick for critical paths dependent on late input X
- Precompute the carry out of each block for both $\text{carry_in} = 0$ and $\text{carry_in} = 1$ (can be done for all blocks in parallel) and then select the correct one by Mux



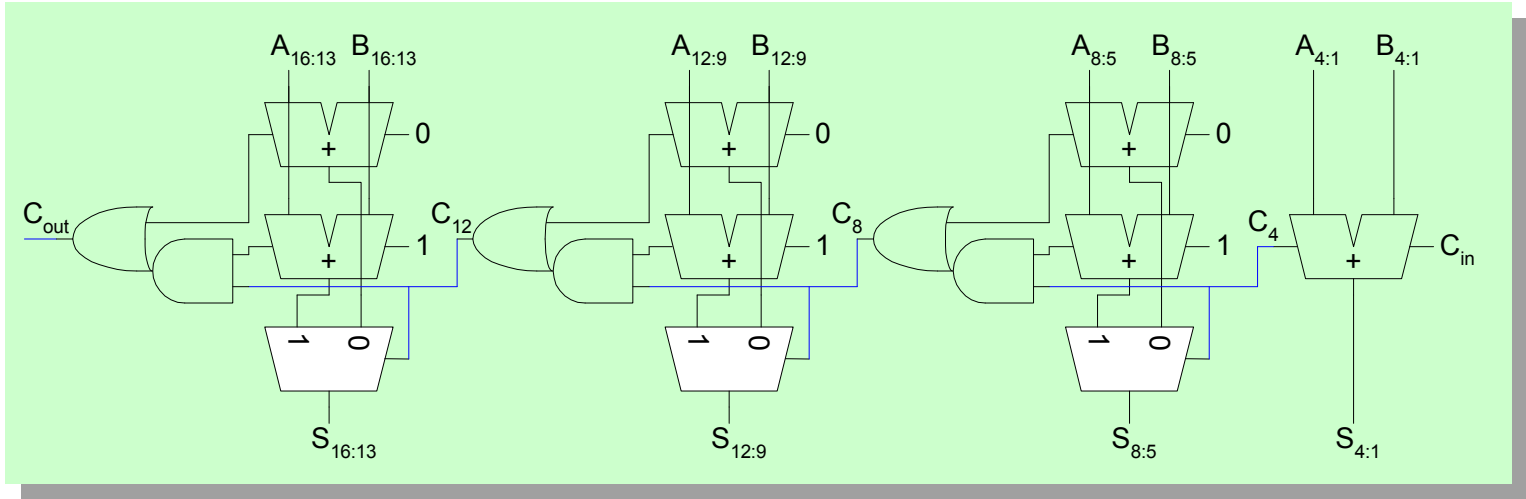


Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**


Adders

► Carry Select Adder (Linear)

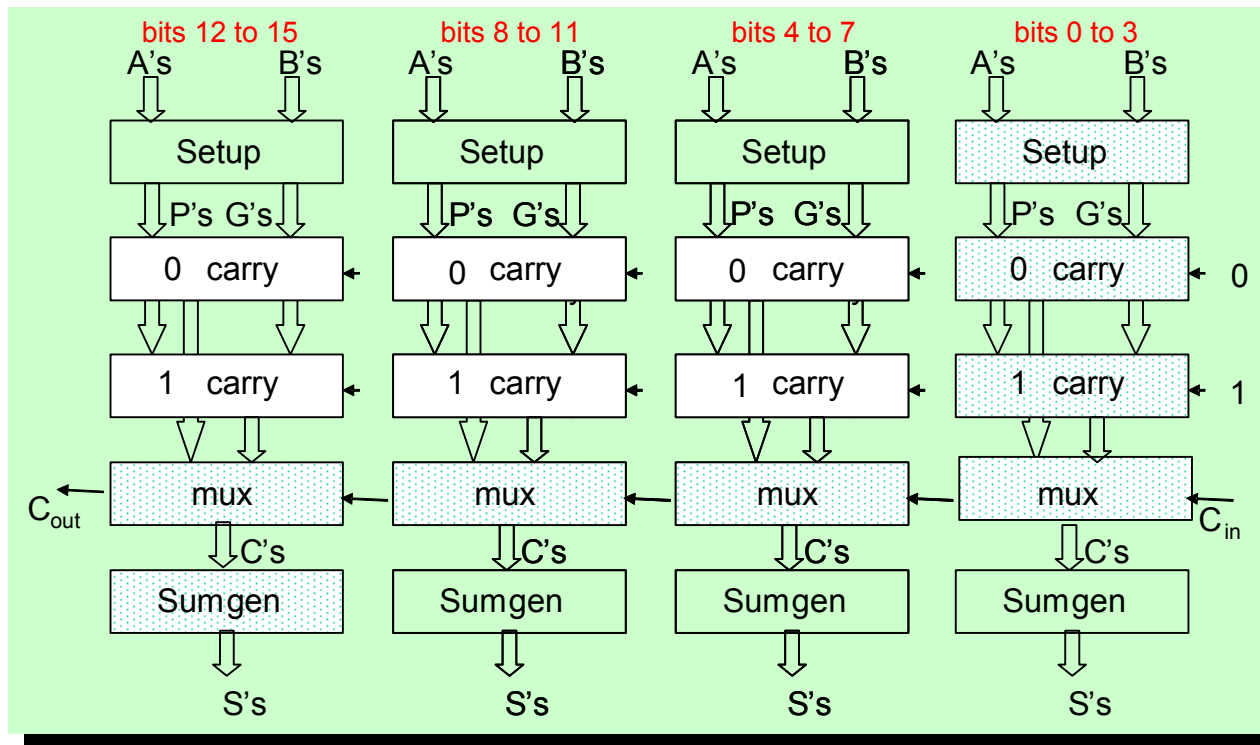

Adders

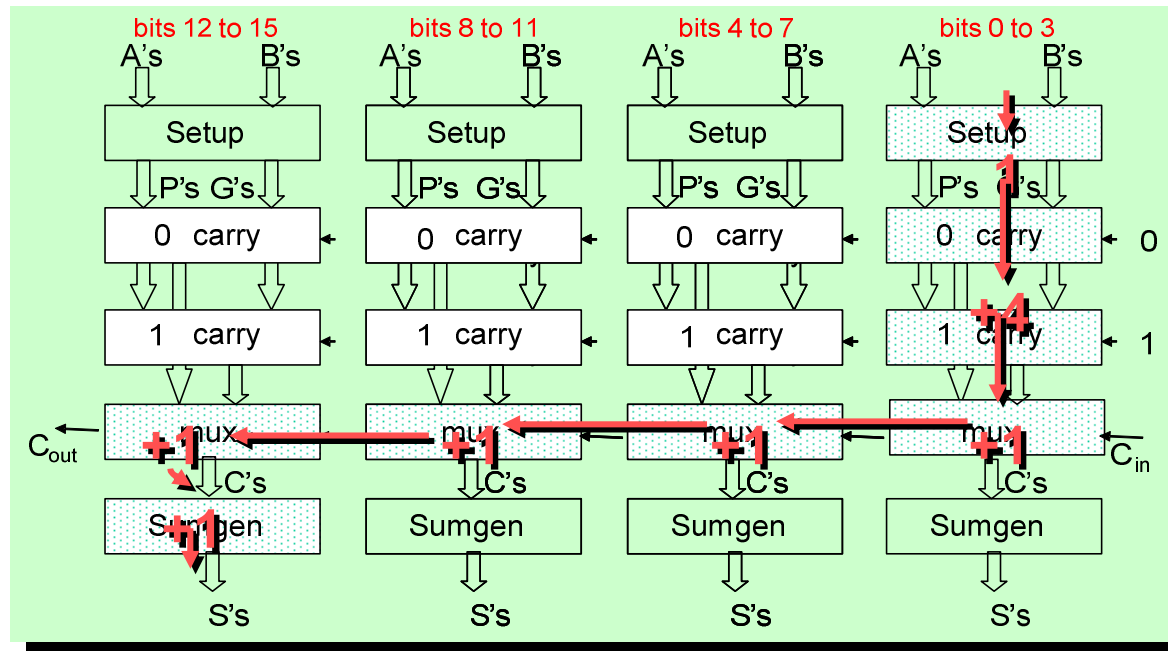► Carry Select Adder (Linear): Critical Path




$$T_{\text{add}} = t_{\text{setup}} + Bt_{\text{carry}} + N/Bt_{\text{mux}} + t_{\text{sum}}$$

Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**


Adders

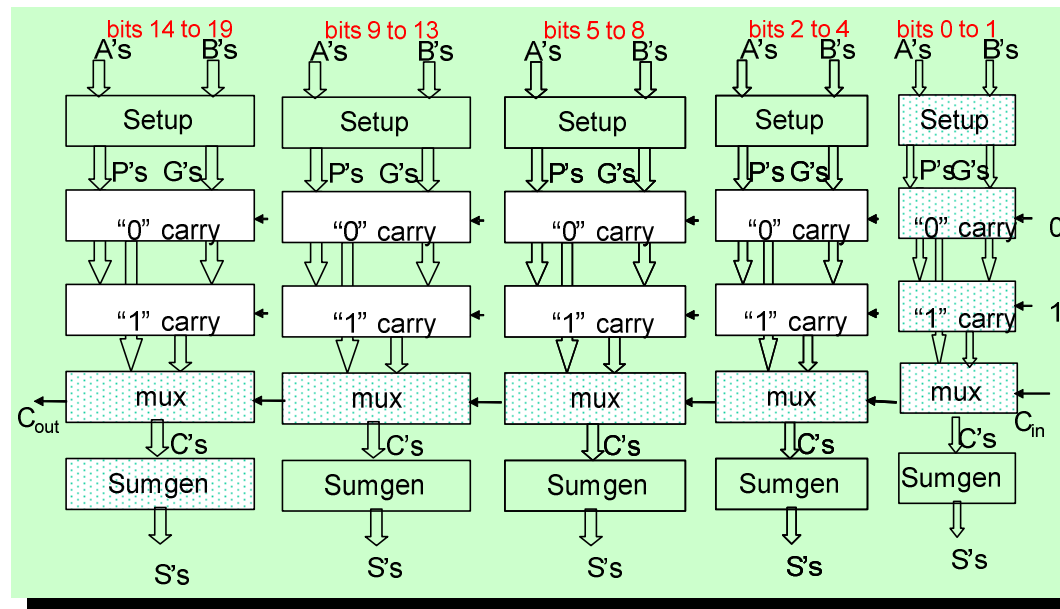- ▶ **Carry Select Adder (Square Root)**
 - ▶ This idea can be carried on in a logarithmic tree fashion to obtain the addition in $\log_2(N)$ time



Adders

► Carry Select Adder (Square Root)

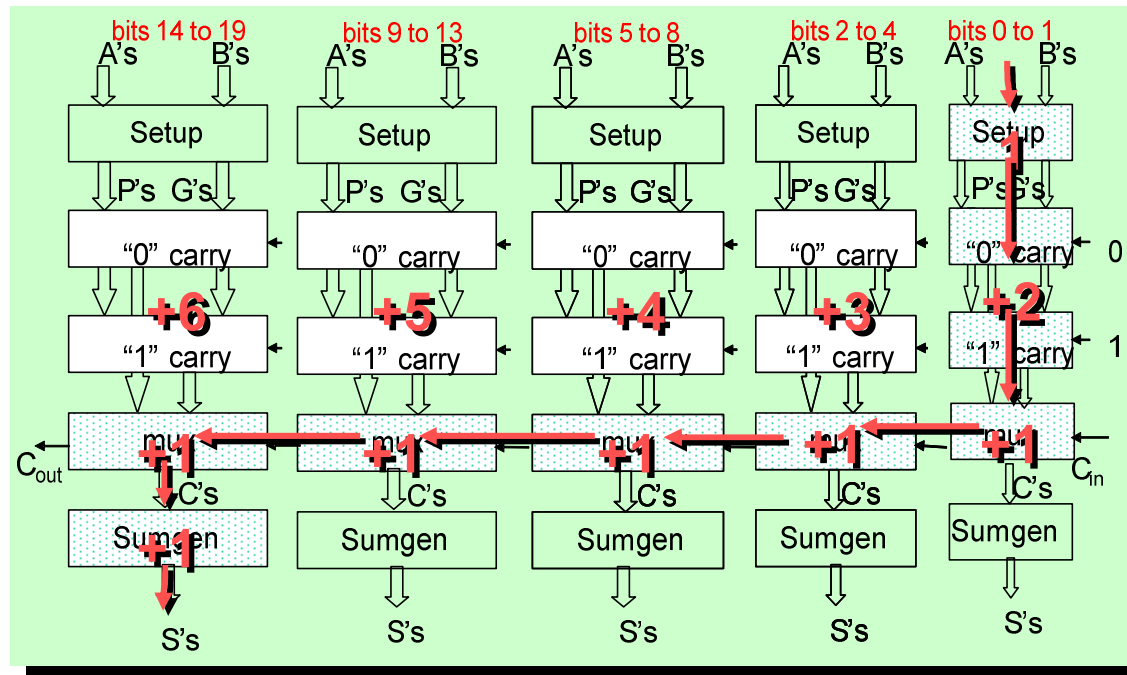


$$T_{\text{add}} = t_{\text{setup}} + 2t_{\text{carry}} + \sqrt{N}t_{\text{mux}} + t_{\text{sum}}$$

Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders

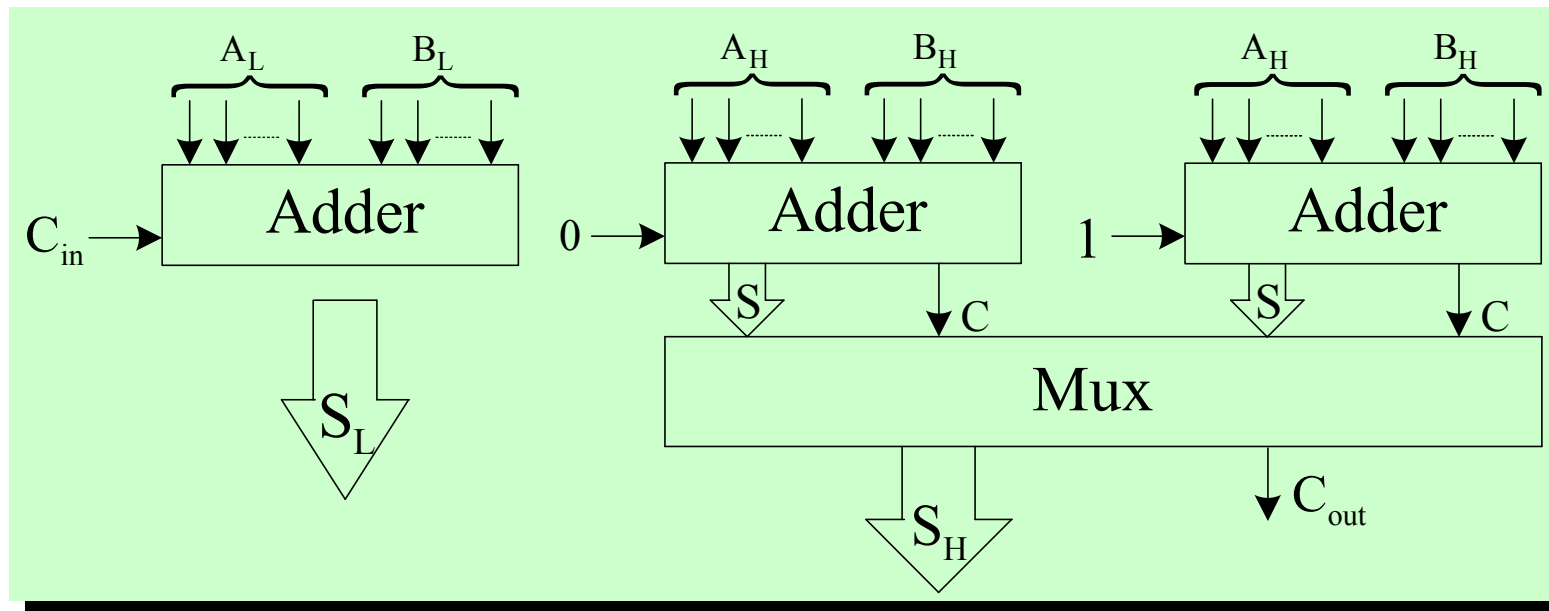- **Conditional Carry Adder**
 - Increase speed twice!





Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders

► Carry Save Adder

 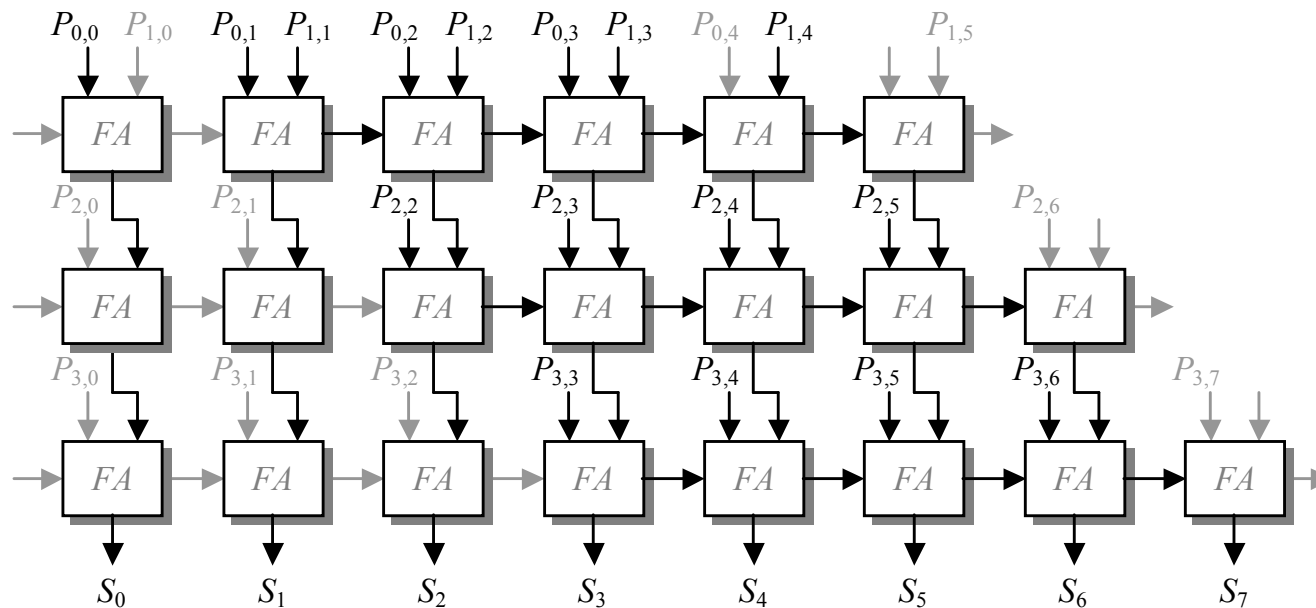
- When adding k n-bit numbers
 - Linear Array (or Tree) Summation



Adders

- ▶ **Carry Save Adder**
 - ▶ When adding k n-bit numbers
 - Tree Summation

CPA
(Carry Propagate Adder)


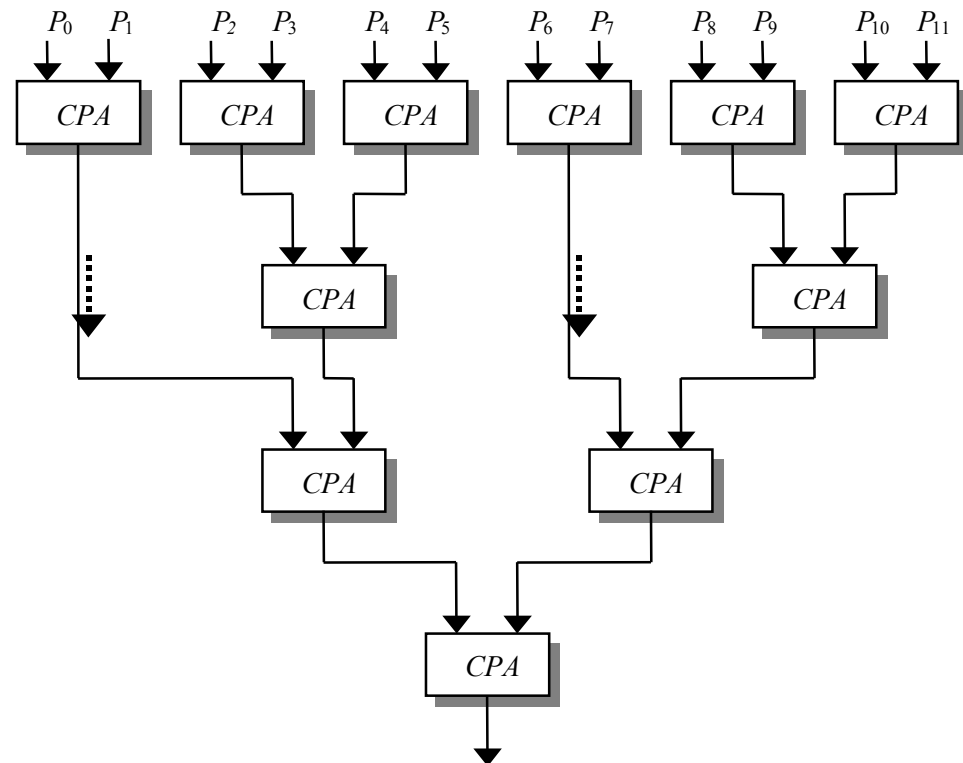


Adders


► Carry Save Adder

► When adding k n-bit numbers

$$\text{CPA:} \\ A + B = S$$

 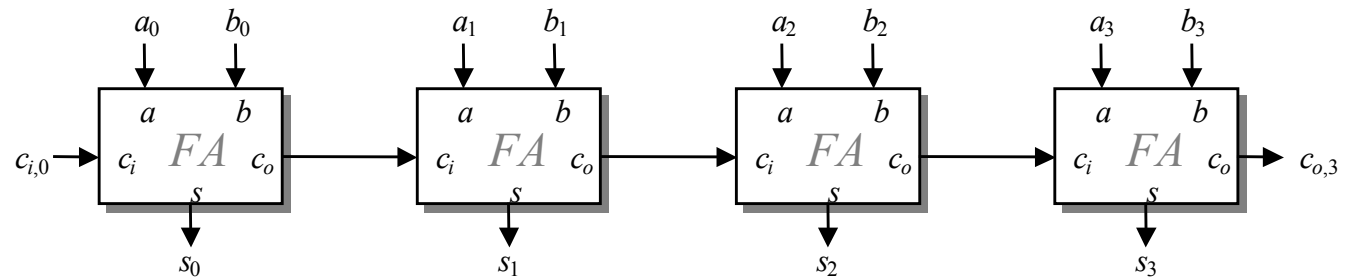


$$\text{CSA:} \\ A + B + C = X + Y$$

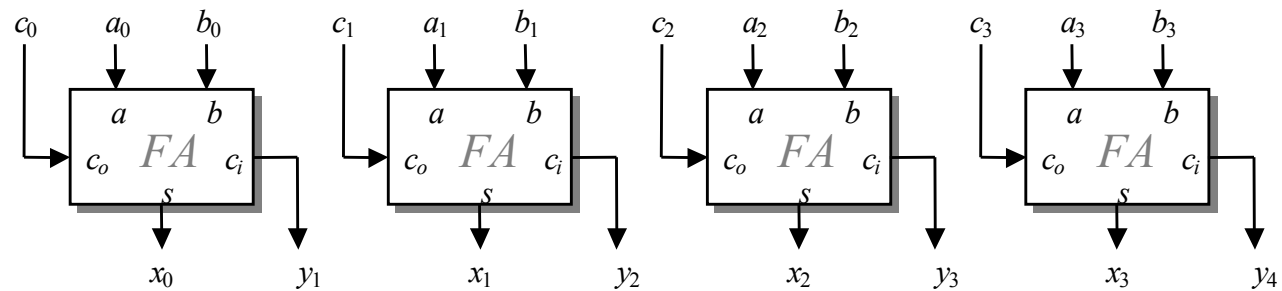

Adders

► Carry-Save Adder


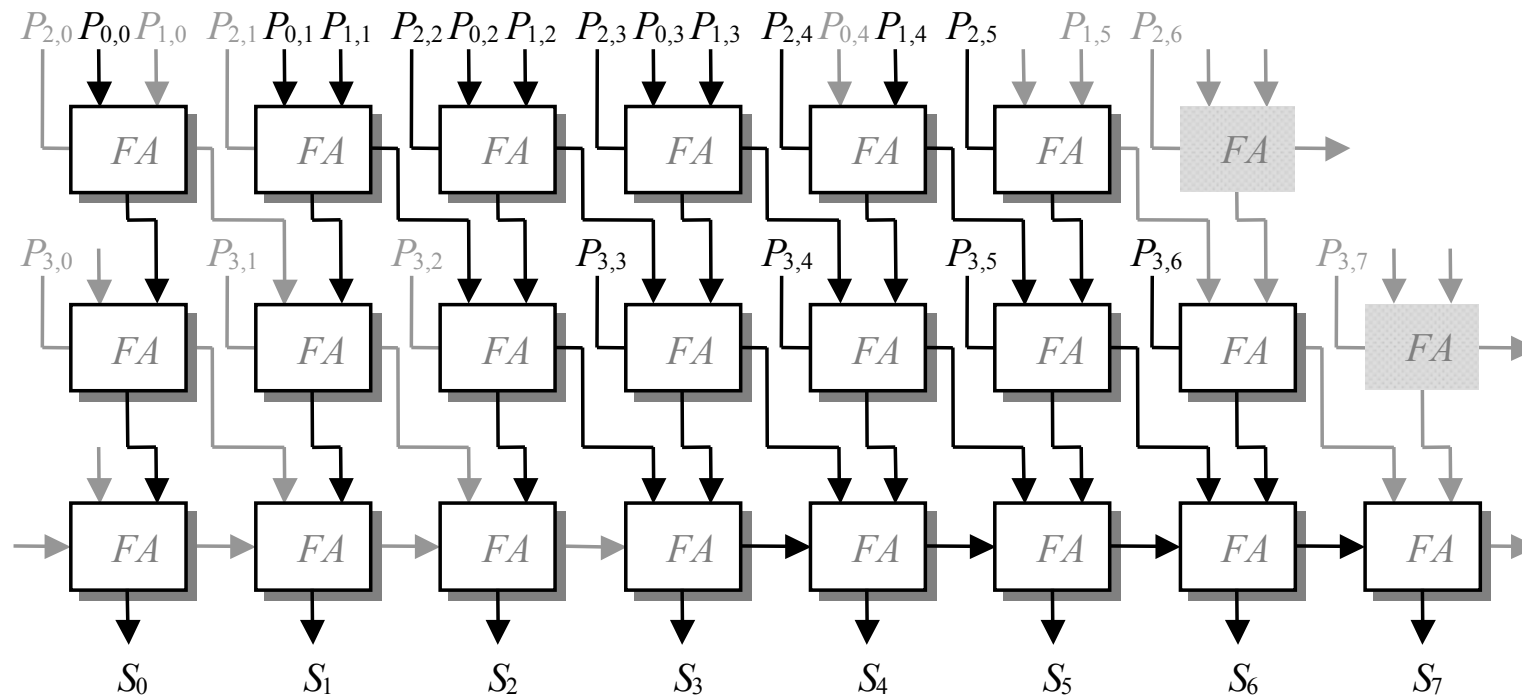


Adders

► Carry Save Adder

► Intermediate FA Cells

  - Better to have the same sum and carry delays (both contribute to critical path)




Adders

- ▶ **Speed up summation with faster adders (Logarithmic)**
 - ▶ Linear (Tree) array has several equal-length critical paths
⇒ All adders need to be replaced
 - ▶ The carry-save array has only ONE critical path
⇒ Replace only the final CPA (see next slide)

Adders

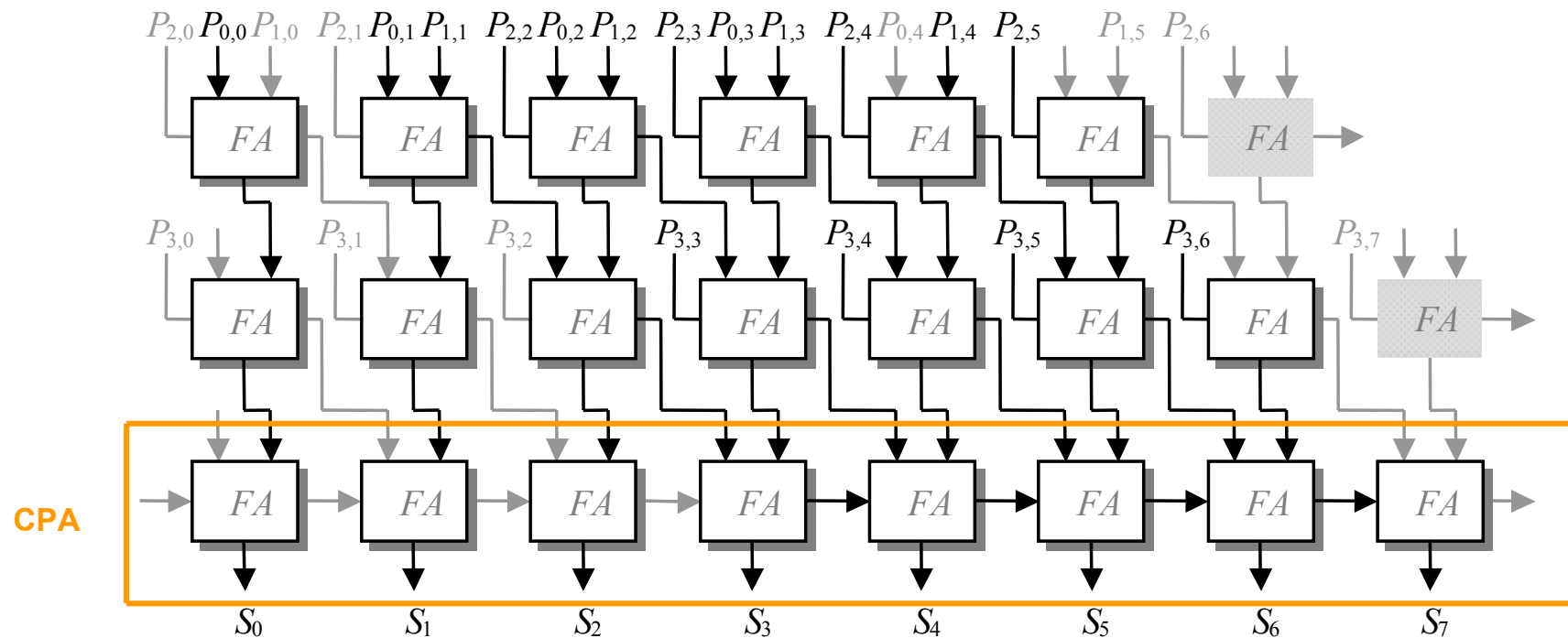- ▶ Speed up summation with faster adders
 - ▶ Replace only the final CPA




Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders

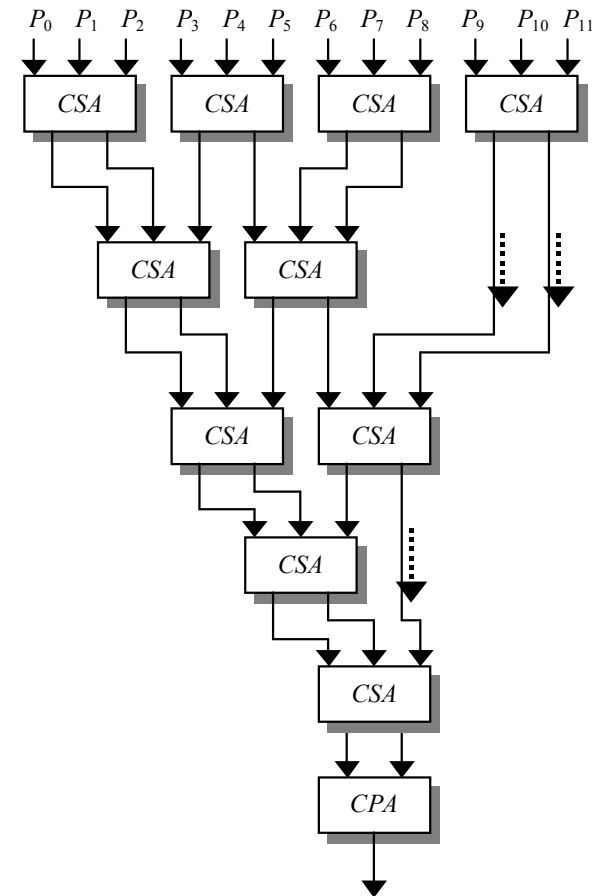- ▶ **Wallace Tree**
 - ▶ Sums in $O(\log m)$ steps




Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders

► LookAhead - Basic Idea

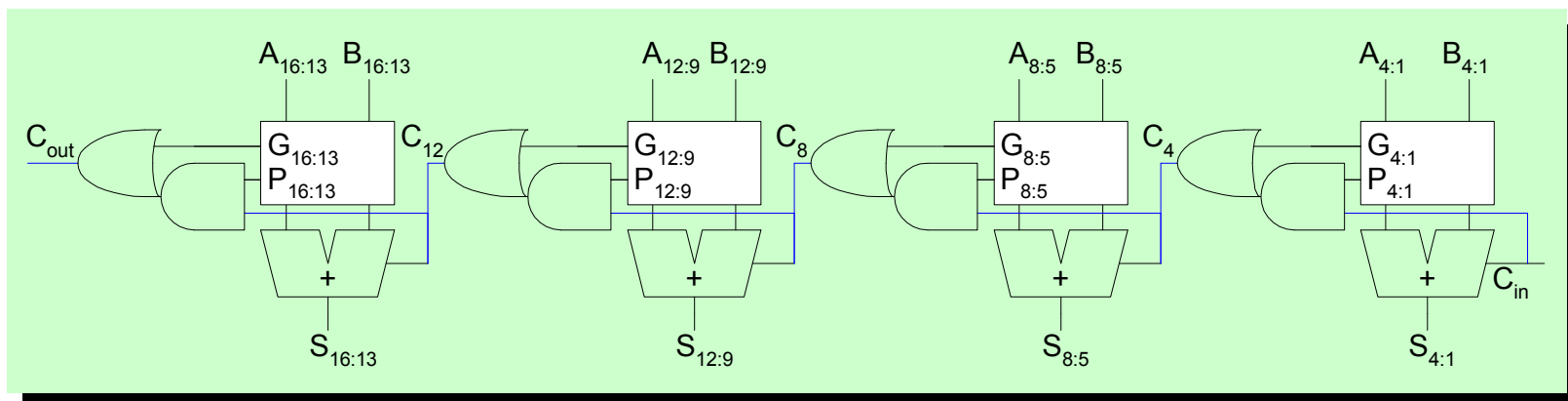
- Carry-lookahead adder computes $G_{i:0}$ for many bits in parallel
- Uses higher-valency cells with more than two inputs



Adders


► LookAhead - Basic Idea

 - $C_1 = G_0 + P_0 C_0$
- $C_2 = G_1 + P_1 G_0 + P_1 P_0 C_0$
- $C_3 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$
- $C_4 = G_3 + P_3 G_2 + P_3 P_2 G_1 + P_3 P_2 P_1 G_0 + P_3 P_2 P_1 P_0 C_0$



Adders

► Look-Ahead: Topology

 

Adders

► Look-Ahead

► Expanding Lookahead equations


- $C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}C_{o,k-2})$

► All the way


- $C_{o,k} = G_k + P_k(G_{k-1} + P_{k-1}(\dots + P_1(G_o + P_oC_{i,o})))$

Adders

► Logarithmic Look-Ahead Adder

 

$$t_p \sim N$$

 

$$t_p \sim \log_2(N)$$

Adders

► Carry Lookahead Trees

$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$

$$C_{o,0} = G_0 + P_0 C_{i,0}$$

$$C_{o,1} = G_1 + P_1 G_0 + P_1 P_0 C_{i,0}$$

$$C_{o,2} = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_{i,0}$$

$$= (G_2 + P_2 G_1) + (P_2 P_1)(G_0 + P_0 C_{i,0}) = G_{2:1} + P_{2:1} C_{o,0}$$


► Can continue building the tree hierarchically

Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders

► Adder Delays - Comparison

 


Contents


- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Adders

► Example: Domino Adder

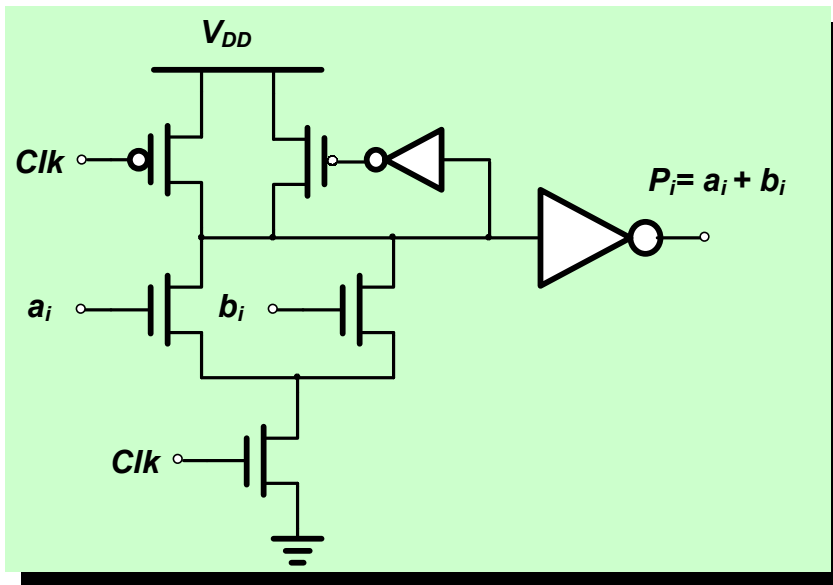


$$\text{Propagate (P)} = A \oplus B$$

 


$$\text{Generate (G)} = AB$$

► Example: Domino Adder

 


Propagate

 

Generate

Adders

► Example: Domino Sum

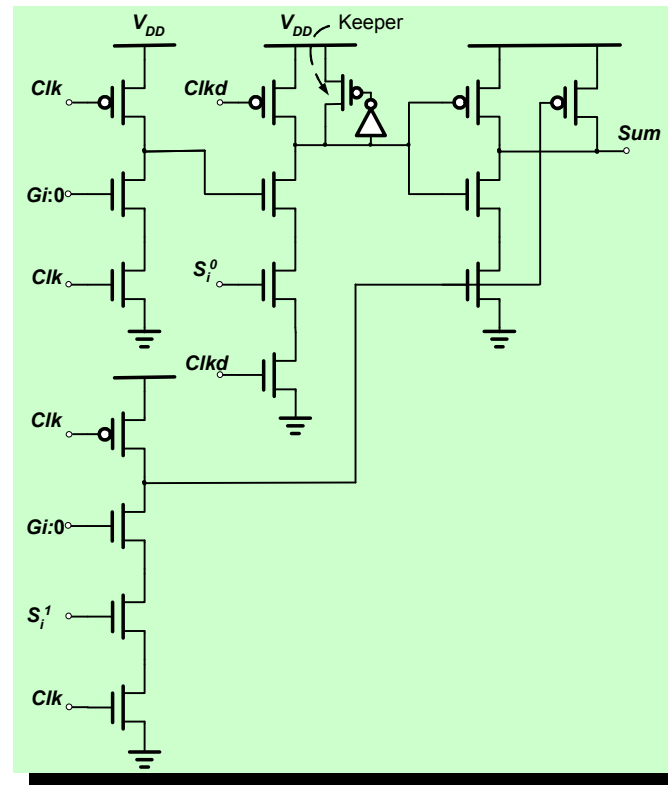

Contents

- ▶ **Outline**
- ▶ **Adders**
 - ▶ **Half Adder**
 - ▶ **Full Adder**
 - **Ripple-Carry Adder (Parallel Adder)**
 - Calculation of Circuit Delays
 - **Carry-Bypass Adder (Carry-Skip Adder)**
 - Manchester Carry Chain (MCC)
 - **Carry Select Adder**
 - Linear
 - Square Root
 - **Conditional Carry Adder**
 - **Carry Save Adder**
 - **Wallace Tree**
 - **Look-Ahead Adder**
- ▶ **Adder Delays - Comparison**
- ▶ **Example**
- ▶ **Summary**

Summary

- ▶ **This lecture describes one of the basic building blocks (Adders) and also implementation of them in transistor level**
- ▶ **Also noted how to choose an adder and designing fast ones**